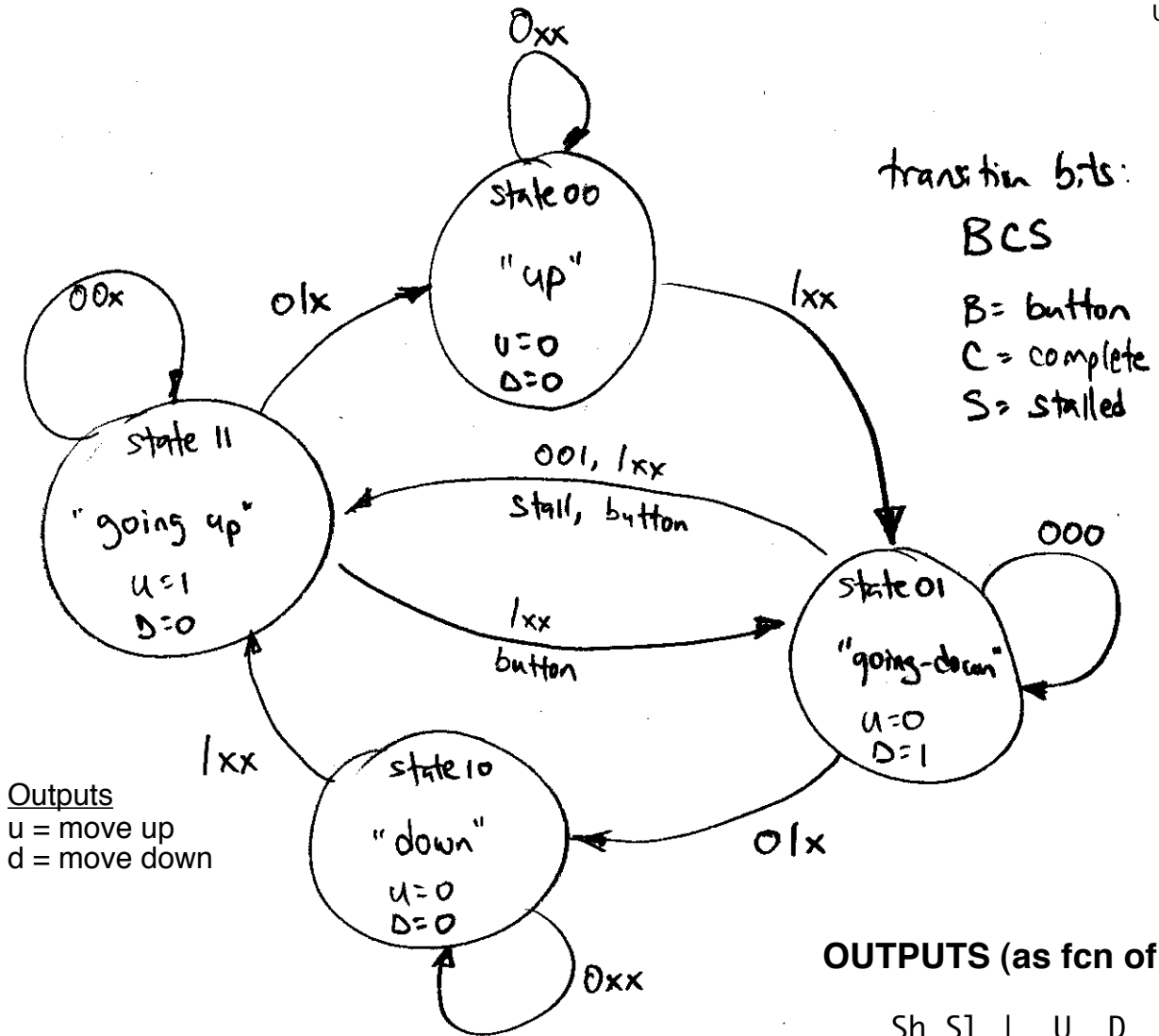


GARAGE DOOR STATE MACHINE



OUTPUTS (as fcn of state)

Sh	Sl	U	D
0	0	0	0
0	1	0	1
1	0	0	0
1	1	1	0

STATE TRANSITION TABLE

Sh	Sl	B	C	S	I	Sh+	Sl+	comment
0	0	0	x	x		0	0	no button
0	0	1	x	x		0	1	button
0	1	0	0	0		0	1	no change
0	1	0	0	1		1	1	stalled, no button
0	1	0	1	x		1	0	no button, complete, maybe stalled too
0	1	1	x	x		1	1	button, maybe stalled or complete
1	0	0	x	x		1	0	no button
1	0	1	x	x		1	1	button
1	1	0	0	x		1	1	no button, not complete, ignore stall
1	1	0	1	x		0	0	complete
1	1	1	x	x		0	1	button override (stall, complete OK)

STATE EQUATIONS & MINIMIZATION

$$S_H^+ = \bar{S}_H S_L \bar{B} \bar{C} S + \bar{S}_H S_L \bar{B} C + \bar{S}_H S_L B + S_H \bar{S}_L \bar{B} + S_H \bar{S}_L B \\ + S_H S_L \bar{B} \bar{C}$$

$$= \bar{S}_H S_L (\bar{B} \bar{C} S + \bar{B} C + B) + S_H \bar{S}_L + S_H S_L \bar{B} \bar{C}$$

$$= \bar{S}_H S_L (\bar{B} (\bar{C} S + C) + B) + S_H (\bar{S}_L + S_L \bar{B} \bar{C})$$

$$S_L^+ = \bar{S}_H \bar{S}_L B + \bar{S}_H S_L \bar{B} \bar{C} \bar{S} + \bar{S}_H S_L \bar{B} \bar{C} S + \bar{S}_H S_L B \\ + S_H \bar{S}_L B + S_H S_L \bar{B} \bar{C} + S_H S_L B$$

$$= \bar{S}_H \bar{S}_L B + \bar{S}_H S_L (\bar{B} \bar{C} + B) + S_H \bar{S}_L B + S_H S_L (\bar{B} \bar{C} + B)$$